
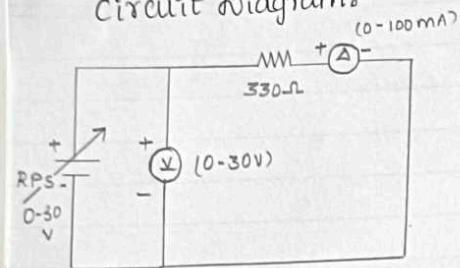


Circuit Diagram:-

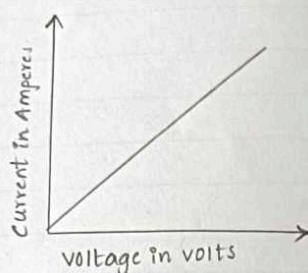

Model Graph:-



Tabulation Values:-

| S.NO | Voltage (V) | current (mA) | Experiment Value $R = V/I \text{ in } \Omega$ | Theoretical Value $R = V/I \text{ in } \Omega$ |
|------|-------------|--------------|--|---|
| 1 | 1 | 5 | 200 | 220Ω |
| 2 | 2 | 10 | 200 | 220Ω |
| 3 | 3 | 16 | 187.5 | 220Ω |
| 4 | 4 | 20 | 200 | 220Ω |
| 5 | 5 | 24 | 208.3 | 220Ω |
| 6 | 6 | 28 | 214.28 | 220Ω |
| 7 | 7 | 32 | 218.75 | 220Ω |

Theoretical Value:- ($V=IR$)

1. $I = V/R = 1/220 = 4.5454 \text{ mA}$; $R = V/I = 1/4.5454 \times 10^{-3} = 220 \Omega$
2. $I = V/R = 2/220 = 9.0909 \text{ mA}$; $R = V/I = 2/9.0909 \times 10^{-3} = 220 \Omega$
3. $I = V/R = 3/220 = 13.6363 \text{ mA}$; $R = V/I = 3/13.6363 \times 10^{-3} = 220 \Omega$
4. $I = V/R = 4/220 = 18.1818 \text{ mA}$; $R = V/I = 4/18.1818 \times 10^{-3} = 220 \Omega$
5. $I = V/R = 5/220 = 22.7272 \text{ mA}$; $R = V/I = 5/22.7272 \times 10^{-3} = 220 \Omega$
6. $I = V/R = 6/220 = 27.2727 \text{ mA}$; $R = V/I = 6/27.2727 \times 10^{-3} = 220 \Omega$
7. $I = V/R = 7/220 = 31.8181 \text{ mA}$; $R = V/I = 7/31.8181 \times 10^{-3} = 220 \Omega$

01: Verification of Ohm's law & Kirchhoff's law

Aim:- To verify ohm's law for a given Resistive Network

Apparatus Required:-

| S.NO | APPARATUS NAME | RANGE | QUANTITY |
|------|--------------------------------|-----------|----------|
| 1. | DC Regulated power supply | 0-30V | 1 |
| 2. | Ammeter | (0-200)mA | 1 |
| 3. | Voltmeter | 0-30V | 1 |
| 4. | Resistor | 1KΩ | 1 |
| 5. | Rheostat | 300Ω/2A | 1 |
| 6. | Bread board & connecting wires | ----- | Required |


Theory: Ohm's law:— Ohm's law states that the current flowing through a conductor is directly proportional to the potential difference across its ends, provided the temperature and physical conditions remains constant. $V=IR$; V = voltage; I = current, R = Resistance.

Procedure:-

1. Make the connections as per circuit diagram.
2. Switch on the power supply to RPS and apply a voltage and take the reading of voltmeter and Ammeter.
3. Adjust the rheostat in steps and take down the reading of Ammeter & voltmeter.
4. Plot a graph with V along x -axis and I along y -axis.
5. The graph will be a straight line which verifies Ohm's law.
6. Determine the slope of the $V-I$ graph. The required slope give resistance of the wire.

Result:- Thus, the Ohm's law is verified for the given circuit.

Circuit diagram:-

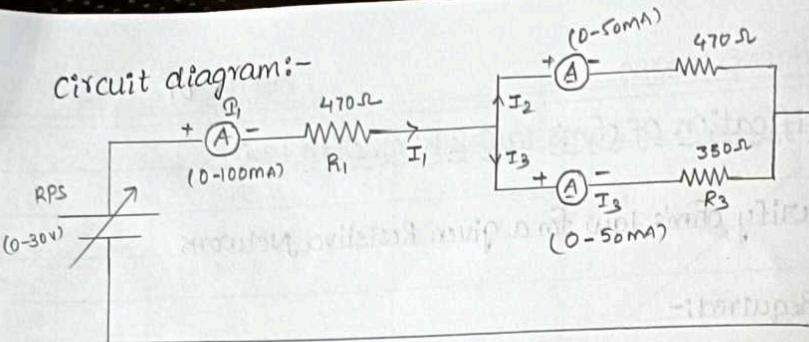

Tabulation:-

| Parameter | Experimental value | | | Theoretical value | | | | | |
|-----------|--------------------|-----------------------------|-----------------------------|-----------------------------|---|-----------------------------|-----------------------------|-----------------------------|---|
| | Supply Voltage | current I ₁ (mA) | current I ₂ (mA) | current I ₃ (mA) | I ₁ = I ₂ + I ₃ (mA) | Current I ₁ (mA) | Current I ₂ (mA) | Current I ₃ (mA) | I ₁ = I ₂ + I ₃ (mA) |
| 10V | 19.5 | 11.5 | 8 | 19.5 | 21.64 | 12.98 | 8.657 | 21.64 | |

Theoretical calculation:-

To find Req:-

$$\text{Req} = R_1 + R_2 \parallel R_3$$

$$= 330 + \left[\frac{330 \times 220}{330 + 220} \right]$$

$$= 330 + 132$$

$$= 462\Omega$$

$$V = 10V$$

$$I_1 = V/R = \frac{10}{462} = 0.02164A = 21.64\text{mA}$$

$$V_1 = I_1 R_1 = 0.02164 \times 330 = 7.14V$$

$$V = V_1 + V_2$$

$$10 = 7.14 + V_2$$

$$V_2 = 2.857V$$

$$I_2 = \frac{V_2}{R_2} = \frac{2.857}{220}$$

$$I_2 = 0.01298 \\ = 12.98\text{mA}$$

$$I_3 = \frac{V_3}{R_3} = \frac{2.857}{330}$$

$$I_3 = 8.657\text{mA}$$

01b. Verification of Kirchhoff's current law.

Aim:- To verify Kirchhoff's current law for the given circuit.

Apparatus Required:-

| S.NO | Apparatus Name | Range | Quantity |
|------|--------------------------------|-----------|----------|
| 1. | DC Regulated power supply | 0-30V | 1 |
| 2. | Ammeter | 0-100mA | 3 |
| 3. | Resistor | 470, 330Ω | 2 |
| 4. | Bread board & connecting wires | - | Required |

Theory:-


Kirchhoff's current law states that the algebraic sum of currents at any junction in an electrical circuit is zero. This means the total current entering a junction is equal to the current leaving junction.

Procedure:-

1. Give the connections as per the circuit diagram.
2. Set a particular value in RPS.
3. Note down the corresponding ammeter reading.
4. Repeat the same for different voltages.

Result:- Thus, the Kirchhoff's current law is verified for a given circuit.

Circuit Diagram:-

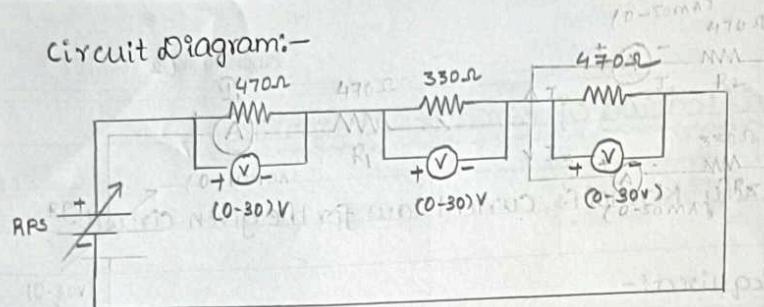

Tabulation:-

↓ (X)-wrong table - (X) ↓

| Parameter | Experimental Value | | | | Theoretical Value | | | | |
|-----------|--------------------|--------------------|--------------------|--------------------|---------------------------------------|--------------------|--------------------|--------------------|-----------------------------|
| | Supply voltage | Current I_1 (mA) | Current I_2 (mA) | Current I_3 (mA) | $\Omega_1 = \Omega_2 + \Omega_3$ (mA) | Current I_1 (mA) | Current I_2 (mA) | Current I_3 (mA) | $\Omega_1 = I_2 + I_3$ (mA) |
| 10V | 19.5 | 11.05 | 8 | 19.5 | 21.64 | 12.98 | 8.657 | 21.64 | 21.64 |

Theoretical calculation:-

$$V = 20V$$

$$R = 330 + 330 + 220 = 880\Omega$$

$$V = I/R = 20/880 = 0.022mA$$

$$V_1 = IR_1 = 0.022 \times 330 = 7.5V$$

$$V_2 = IR_2 = 0.022 \times 330 = 7.5V$$

$$V_3 = IR_3 = 0.022 \times 220 = 5V$$

$$V = V_1 + V_2 + V_3 \Rightarrow 7.5 + 7.5 + 5 = 20V$$

$$V = 10V$$

$$R = R_1 + R_2 + R_3$$

$$R = 330 + 330 + 220 \Rightarrow 880\Omega$$

$$V = I/R = 10/880 \Rightarrow 0.011A$$

$$V_1 = I_1 R_1 = 0.011 \times 330 \Rightarrow V_1 = 3.65V$$

$$V_2 = I_2 R_2 = 0.011 \times 330 \Rightarrow V_2 = 3.65V$$

$$V_3 = I_3 R_3 = 0.011 \times 220 \Rightarrow V_3 = 2.42V$$

$$\therefore V = V_1 + V_2 + V_3 \Rightarrow 3.65 + 3.65 + 2.42$$

$$V = 9.72V$$

Tabulation:-

| Supply voltage | Theoretical value | | | | Experimental value | | | |
|----------------|-------------------|--------|-------|------------------------------|--------------------|-------|-------|------------------------------|
| | V_1 | V_2 | V_3 | KVL $V = V_1 + V_2 + V_3$ | V_1 | V_2 | V_3 | KVL $V = V_1 + V_2 + V_3$ |
| 20V | 7.5V | 7.5V | 5 | 20V | 7.2 | 7.3 | 4.5 | 21 |
| 10V | 9.72V | 12.84V | 8.65V | 21.64V | 3.5 | 3.3 | 2.42 | 9.72 |

Kirchoff's voltage law

(C)

Aim:- To verify Kirchoff's voltage law for the given circuit.

Apparatus required:-

| S.NO. | Apparatus Name | Range | Quantity |
|-------|--------------------------------|-----------------|----------|
| 1. | DC Regulated power supply | 0-30V | 2 |
| 2. | Voltmeter | 0-30V | 3 |
| 3. | Resistor | 1KΩ, 220Ω, 330Ω | Each one |
| 4. | Bread board & connecting wires | - | Required |

Theory:-

Kirchoff's Voltage Law (KVL) states that the sum of the all voltages around a closed loop in a circuit is always equal to zero.


Procedure:-

- Give the connections as per the circuit diagram.
- Set a particular value in the RPS.
- Note the corresponding voltage readings.
- Repeat the same for different voltage.

Result:-

Thus, the Kirchoff's Voltage law is verified for given circuit.

Circuit diagram:-

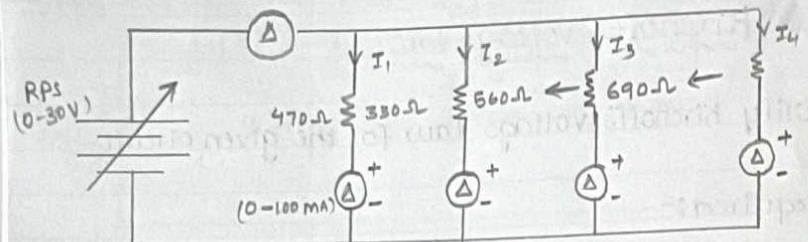

Tabulation values:-

| S.NO | Voltage | Current (mA) | | | |
|------|---------|----------------|----------------|----------------|----------------|
| | | I ₁ | I ₂ | I ₃ | I ₄ |
| 1. | 5 | 5 | 10.64 | 15.15 | 8.03 |
| 2. | 10 | 10 | 21.28 | 30.3 | 17.86 |
| 3. | 15 | 15 | 31.91 | 45.45 | 26.79 |
| 4. | 20 | 20 | 42.55 | 60.61 | 35.71 |
| 5. | 25 | 25 | 53.19 | 75.76 | 44.64 |

Calculation:-

$$\text{For voltage } (V) = 5\text{V}$$

$$\text{Resistor } (R_1) = 470\text{k}\Omega$$

$$R \cdot I_1 = V/R_1 = 5/470 = 10.64\text{mA}$$

$$R_2 = 330\text{k}\Omega$$

$$I_2 = V/R_2 = 5/330 = 15.15\text{mA}$$

$$R_3 = 560\text{k}\Omega$$

$$I_3 = V/R_3 = 5/560 = 8.03\text{mA}$$

$$R_4 = 690\text{k}\Omega$$

$$I_4 = V/R_4 = 5/690 = 7.2\text{mA}$$

For Voltage (V) = 15V

$$R_1 = 470\text{k}\Omega$$

$$I_1 = V/R_1 = 3.19\text{mA}$$

$$R_2 = 330\text{k}\Omega, I_2 = V/R_2 = 45.45\text{mA}$$

$$R_3 = 560\text{k}\Omega$$

$$I_3 = 15/560 = 26.77\text{mA}$$

$$I_4 = V/R_4 = 15/690 = 21.74\text{mA}$$

For Voltage (V) = 10V

$$R_1 = 470\text{k}\Omega, R_2 = 330\text{k}\Omega, R_3 = 560\text{k}\Omega, R_4 = 690\text{k}\Omega$$

$$I_1 = V/R_1, I_2 = V/R_2, I_3 = 17.86 \text{ mA}, I_4 = 14.47\text{mA}$$

$$I_1 = 21.28\text{mA}, I_2 = 30.3\text{mA}$$

For Voltage (V) = 20V

$$R_1 = 470\text{k}\Omega, I_1 = 20/470 = 42.55\text{mA}$$

$$R_2 = 330\text{k}\Omega, I_2 = 20/330 = 60.61\text{mA}$$

$$R_3 = 560\text{k}\Omega, I_3 = 35.71\text{mA}$$

$$R_4 = 690\text{k}\Omega, I_4 = 44.64\text{mA}$$

Q2: Verification of current and voltage Division Rules.

Aim:- To calculate the individual branch currents and total current drawn from the power supply using current and voltage division rules.

Apparatus Required:-

| S.NO. | Apparatus NAME | Range | Quantity |
|-------|-------------------------------|-----------|----------|
| 1. | DC Regulated power supply | 0-30V | 1 |
| 2. | Ammeter | 0-200mA | 4 |
| 3. | Resistor | 1kΩ, 220Ω | Each two |
| 4. | Breadboard & connecting wires | - | Required |

Theory:-

The voltage division rule states that in a series circuit, the voltage across a resistor is proportional to its resistance. The current division rule states that in a parallel circuit, inversely proportional to resistance.

Procedure:-

1. Give the connections as per the circuit diagram.


2. Set a particular value in RPS.

3. Note down the corresponding ammeter reading.

4. Repeat the same for different voltages.

Result:- Thus power supply is calculated using current & voltage division rules.


circuit diagram:-

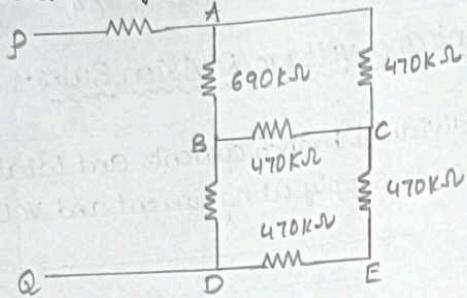

Tabulation:-

| S.NO. | Theoretical value (R _{PQ} in ohm) | Measured Value (R _{PQ} in ohm) |
|-------|---|--|
| 1. | 2.97kΩ | 2.97kΩ |


calculation:-

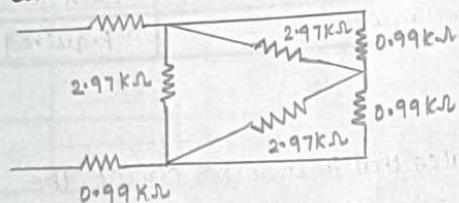


$$R_{AB} = \frac{R_A R_B C}{R_A + R_B + R_C} = \frac{2.97 \times 0.99 \times 0.99}{2.97 + 0.99 + 0.99} = 0.99\text{k}\Omega$$

$$R_{BC} = \frac{R_A B + R_B C + R_C A}{R_A} = \frac{2.97 + 0.99 + 0.99}{2.97} = 2.97\text{k}\Omega$$

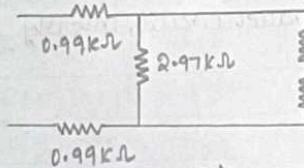
$$R_{CA} = \frac{R_A B + R_B C + R_C A}{R_B} = 2.97\text{k}\Omega$$


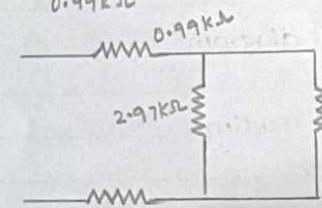
$$\frac{0.99 \times 2.97}{0.99 + 2.97} = 0.7425\text{k}\Omega$$


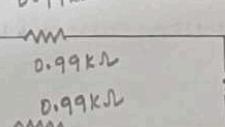
$$0.7425 + 0.7425 = 1.485\text{k}\Omega$$



$$\frac{(2.97 \times 1.485) \times 10^6}{(2.97 \times 1.485) \times 10^3} = 0.99\text{k}\Omega$$

$$Req = (0.99 + 0.99 + 0.99) \times 10^3 \Rightarrow 2.97\text{k}\Omega$$

03. Verification of star-delta transformation.

Aim:- To calculate the equivalent circuit resistance using star-delta transformation technique.

Apparatus Required:-

| S.NO | APPARATUS NAME | RANGE | QUANTITY |
|------|----------------|-------|----------|
| 1. | Resistor | - | Required |
| 2. | Bread board | - | Required |


procedure:-

1. Give the connections as per the circuit diagram.
2. Determine the equivalent resistance of the circuit between P and Q using star-delta transformation technique.
3. Verify the same by connecting multimeter across PQ.

Result:-

Thus, the equivalent circuit resistance is obtained using star-delta transformation, technique.

Circuit Diagram:-

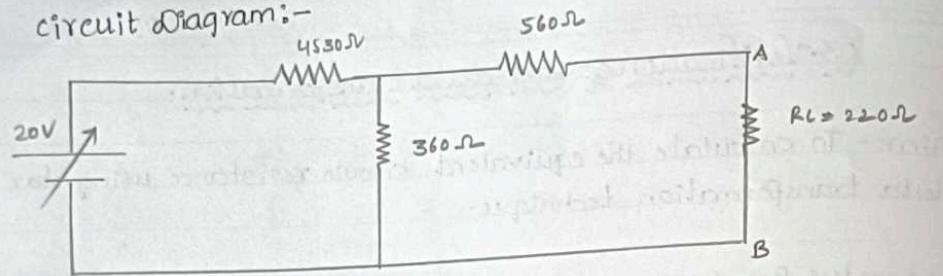

Tabulation:-

| Supply Voltage | Theoretical Values | | | Experimental Values | | |
|----------------|--------------------|-----------------|----------------|---------------------|-----------------|----------------|
| | R _{Th} | V _{th} | P _L | R _{Th} | V _{th} | P _L |
| 20V | 2421.4 | 8.2 | 3.3 | 2401 | 7.5 | 3.1 |

Calculation:-

$$R_{Th} = \frac{4530 + 3160}{4530 + 3160}$$

$$\therefore R_{Th} = 2421.48 \Omega$$



$$V_{th} = \frac{20 \times 3160}{4530 + 3160}$$

$$= \frac{63200}{7690}$$

$$\therefore V_{th} = 8.21 V$$

$$P_L = \frac{8.21}{2421.48 + 220}$$

$$\therefore I_L = 0.0031 A$$

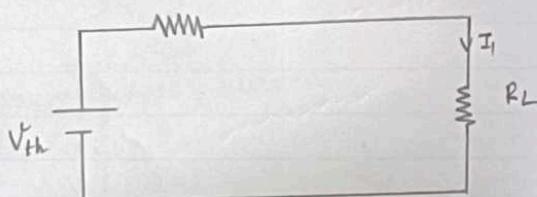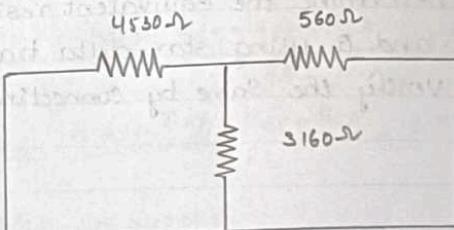

04. Verification of Thevenin's theorem and Norton's theorem.

Aim:- To verify the equivalent circuit parameters of Thevenin's and Norton's theorems theoretically and practically.


Apparatus Required:-

| S.NO. | APPARATUS NAME | Range | Quantity |
|-------|-------------------------------|-----------------------------|----------|
| 1. | DC Regulated power supply | 0-30V | 1 |
| 2. | Voltmeter | 0-30V | 1 |
| 3. | Ammeter | (0-200) mA | 1 |
| 4. | Resistor | 330Ω, 220Ω, 47Ω, 560Ω, 100Ω | Required |
| 5. | Multimeter | - | 1 |
| 6. | Breadboard & connecting wires | - | Required |

Procedure:-

1. Give the connections as per circuit diagram.
2. Measure R_{Th} using a multimeter by killing sources (O.c the current source and s.c the voltage source) and open-circuit R_L.
3. Measure V_{th} across A and B (open circuit R_L)
4. Measure load current I_L through R_L.
 $I_L = V_{th} / R_{Th} + R_L$
5. Draw the Thevenin's Equivalent circuit.

Circuit Diagram:-

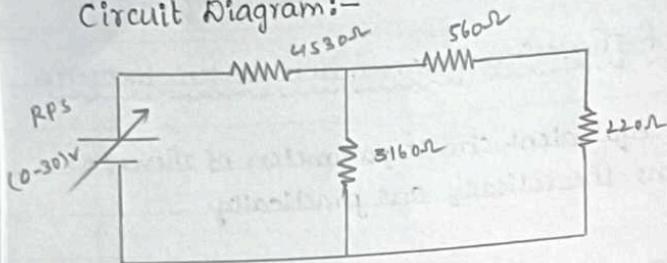

Popular observations:-

| Supply Voltage | Theoretical Values | | | Measured values | | |
|----------------|--------------------|---------------|------------|-----------------|---------------|------------|
| | R_{Th} | I_{SC} (mA) | I_L (mA) | R_{Th} | I_{SC} (mA) | I_L (mA) |
| 20 | 2421.48 | 3.3 | 3.0 | 2421.48 | 3.3 | 3.1 |

Calculations:-

$$R_{Th} = \frac{4530 \times 3160}{4530 + 3160}$$

$$R_{Th} = 2421.48 \Omega$$

$$Req^o = \frac{4530 + 560 \times 3160}{360 + 3160}$$

$$Req^o = 5005.69 \Omega$$

$$I_T = \frac{20}{5005.69}$$



$$I_T = 0.00019 A$$

$$I_{SC} = \frac{I_T \times 3160}{560 + 3160}$$

$$= 0.003312 A$$

$$I_L = \frac{I_{SC} \times R_{Th}}{R_{Th} + R_L}$$

$$\therefore I_L = 0.00303 A.$$

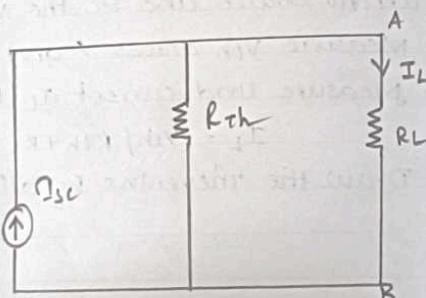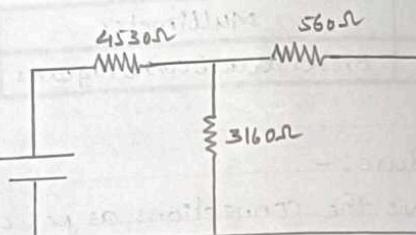


procedure:- [Norton's theorem].

1. Give the connections as per circuit diagram
2. Measure R_{Th} using a multimeter by killing sources [O.c the current source and S.c the voltage source] and open circuit R_L .
3. Measure load current I_L through R_L .
4. Measure I_T through A and B.
5. Draw the NORTON'S EQUIVALENT circuit.

Result:-

Thus, the equivalent circuit parameters are obtained using Thevenins and Norton's theorem.

Circuit Diagram:-

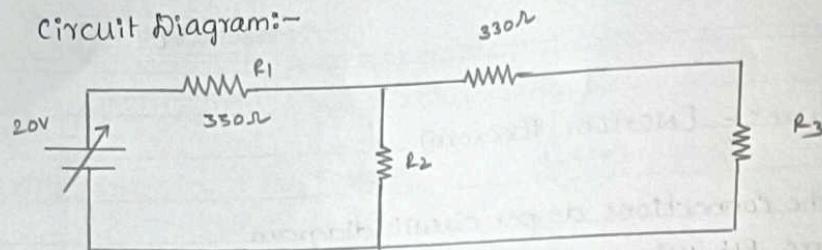

Tabular observations:-

| Supply Voltage | Theoretical values | | | Measured value | | | Max. Power (W) |
|----------------|---------------------|---------------------|---------------------|---------------------|---------------------|---------------------|----------------|
| | R _{Th} (Ω) | V _{th} (V) | I _L (mA) | R _{Th} (Ω) | V _{th} (V) | I _L (mA) | |
| 20V | 462 | 8 | 12 | 448 | 7.5 | 11.8 | 0.0306W |

Theoretical calculation:-

$$R_{Th} = \frac{330 + \frac{830 \times 220}{330 + 220}}{330 + 220}$$

$$R_{Th} = 462 \Omega$$

$$V_{th} = \frac{20 \times 220}{330 + 220}$$

$$V_{th} = 8V$$

$$I_L = \frac{V_{th}}{R_{Th} + R_L}$$

$$I_L = 12 \text{ mA}$$

P_{max} calculation:-

$$\frac{V_{th}^2}{4R_{Th}} = \frac{8^2}{4 \times 462} = 0.0346 \text{ W}$$

Page No. 08

05. Verification of Max. power Transfer theorem and Superposition theorem

5a. Max. power Transfer theorem:-

Aim:- To verify maximum power transfer theorem.

Apparatus Required :-


| SNO. | Apparatus Name | Range | Quantity |
|------|-------------------------------|------------|----------|
| 1. | DC Regulated power supply | 0-30V | 1 |
| 2. | Voltmeter | 0-30V | 1 |
| 3. | Ammeter | 0-200mA | 1 |
| 4. | Resistor | 330Ω, 220Ω | Each two |
| 5. | Multimeter | - | 1 |
| 6. | Breadboard & connecting wires | | Required |

procedure:-

1. Give the connections as per the circuit diagram.
2. Measure the R_{th} using a multimeter.
3. Measure the V_{th} across 220Ω (R_L).
4. Measure load current (I_L) through R_L.
5. calculate the maximum power transferred to the load.

Result:- Thus, the maximum power transfer theorem is verified.

Circuit diagram:-

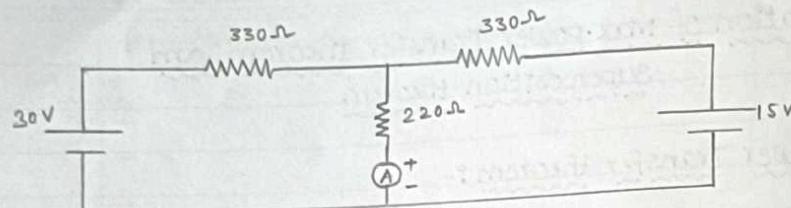

Parabolic calculation:

| Meas- urement | calculated current | | Measured current | | Net Current (mA) |
|------------------|--------------------|-------|------------------|-------|------------------------|
| | V=20V | V=15V | V=20V | V=15V | |
| 45.2 | 25.8 | 19.4 | 27.2 | 19.5 | 46.8 |

$$V = 20V$$

$$\begin{aligned} R_{eq} &= 330 + 132 \\ &= 462\Omega \end{aligned}$$

$$I = \frac{20}{462} = 43mA$$

$$I_L' = 25.8\text{ mA}$$

$$V = 18V$$

$$R_{eq} = 462\Omega$$

$$I = \frac{18}{462} = 32.4\text{ mA} \Rightarrow I_L'' = 19.4\text{ mA}$$

$$I_L = I_L' + I_L''$$

$$= 25.8 + 19.4$$

$$= 45.2\text{ mA}$$

5b. Superposition Theorem:-

Aim:- To determine the current flow through the load Resistor using superposition theorem.

Apparatus Required:-

| S.NO. | Apparatus name | Range | Quantity |
|-------|-------------------------------|-----------------|----------|
| 1. | DC Regulated power supply | 0-30V | 2 |
| 2. | Voltmeter | 0-30V | 1 |
| 3. | Ammeter | 0-200mA | 1 |
| 4. | Resistor | 1kΩ, 220Ω, 330Ω | Each-1 |
| 5. | Multimeter | - | 1 |
| 6. | Breadboard & connecting wires | - | Required |

Procedure:-

1. Give the connections as per circuit
2. Measure current flow through $1k\Omega$ by connecting both supplies
3. Short circuit 20V source
4. Measure current flow through $1k\Omega$ by the connecting 20V supply
5. Short circuit 15V source
6. Measure current flow through $1k\Omega$ by connecting 15V supply
7. Verify the net current through $1k\Omega$ resistor.

Result:- Thus, the current flow through the load resistor using Superposition theorem.

Model Calculations:-

| S.No | Load current (I_2) | Secondary voltage (V_2) | Primary voltage (V_1) | Primary current (I_1) | Power output | Efficiency power input ($P_o/P_i\%$) | Voltage Regulation ($\% \delta$) |
|------|------------------------|-----------------------------|---------------------------|---------------------------|--------------|--|------------------------------------|
| 1. | 0 | 230 | 230 | 0 | 0 | 0 | $\frac{230 - 230}{230} = 0$ |
| 2. | 0.3 | 220 | 228 | 1 | 200 | 94.3 | $\frac{230 - 220}{220} = 4.5\%$ |
| 3. | 0.8 | 216 | 228 | 1.8 | 180 | 96 | $\frac{230 - 216}{216} = 6.4\%$ |
| 4. | 2.1 | 212 | 224 | 2.6 | 720 | 97.2 | $\frac{230 - 212}{212} = 8.4\%$ |
| 5. | 3 | 208 | 224 | 3.4 | 940 | 98.9 | $\frac{230 - 208}{208} = 10\%$ |

Q6. Load test on single phase transformer

Aim:- To Evaluate the transformer performance under full load conditions.

Apparatus Required:-

| S.NO. | Apparatus Name | Range | Quantity |
|-------|--------------------------|----------|----------|
| 1. | Single phase transformer | 1φ | 1 |
| 2. | Voltmeter | 0-50V | 1 |
| 3. | Ammeter | 0-300V | 1 |
| 4. | Supply source | 0-10A | 1 |
| 5. | Load Bank | 5kW-230W | 1 |
| 6. | Watmeter | - | 1 |

Theory:-

A load test on a single phase transformer is used to determine its efficiency and voltage regulation under various load conditions. The test measures parameters such as power loss, output voltage and current.


Procedure:-

1. Connect the primary winding of the transformer to the AC power source.
2. Connect the secondary winding to load bank.
3. Connect the voltmeter across the secondary winding to measure the Secondary Voltage.

Model calculation

$$\text{Efficiency} = \frac{P_{\text{output}}}{P_{\text{input}}} \times 100$$
$$= \frac{200}{212} \times 100$$
$$= 94.3\%$$

Circuit Diagram:-

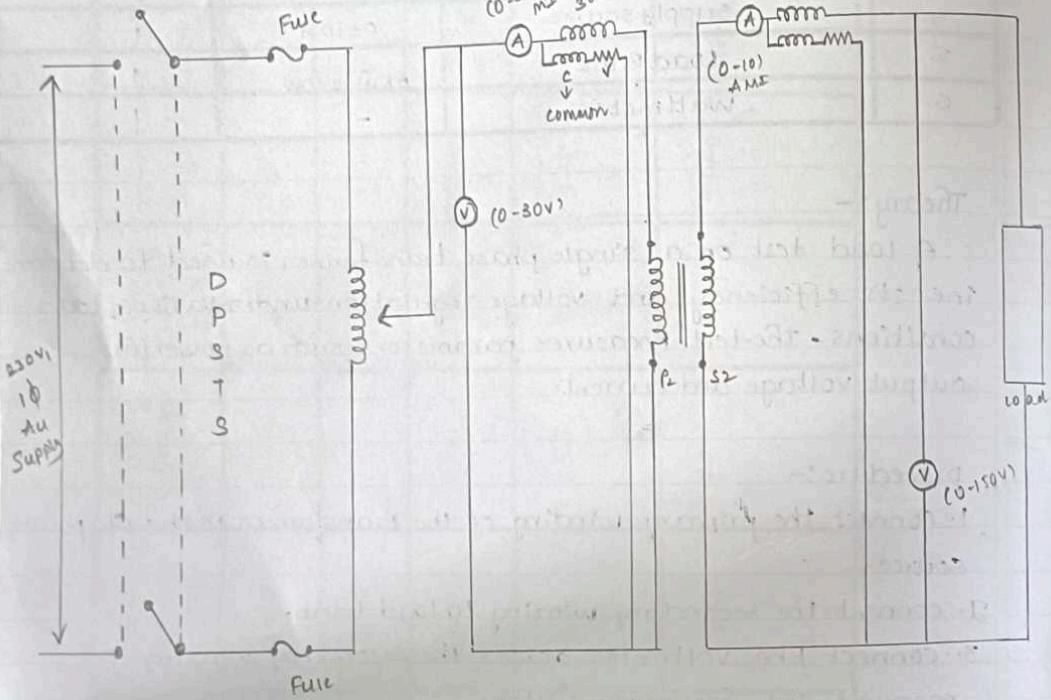

$$\text{Voltage Resolution} = \frac{\sqrt{V_{\text{no load}}} - \sqrt{V_{\text{full load}}}}{V_{\text{full load}}} \times 10$$
$$= \frac{230 - 220}{220} \times 100$$
$$= 4.5\%$$

Page No. 11

Adjust the load:-

1. Start the no. load on the secondary side and gradually increase the load by adjusting variables.
2. Increasing the load until the rated current flows through the winding.
3. Record readings. [V₁, V₂, I₁, T₂, and P]
4. calculate Efficiency.

Result:- Thus, the load test on single phase transformer is conducted.

observation:-

open circuit Rated voltage.

| V | A | W (Experiment) | W (Theoretical) |
|-----|-----|---------------------|----------------------|
| 230 | 0.3 | 64 | 69 |

short circuit Rated voltage.

| V | A | W (Experiment) | W (Theoretical) |
|----|-----|---------------------|----------------------|
| 24 | 4.2 | 76 | 100.8 |


calculation:

$$P = V$$


$$P = 230 \times 0.3$$

$$P = 69W$$

Circuit Diagram :-

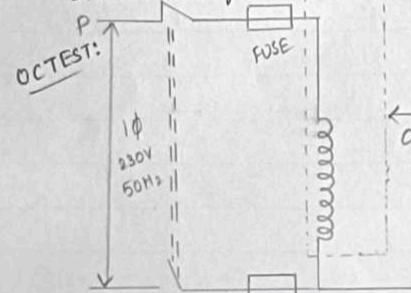

SC TEST: N 1 phase variac

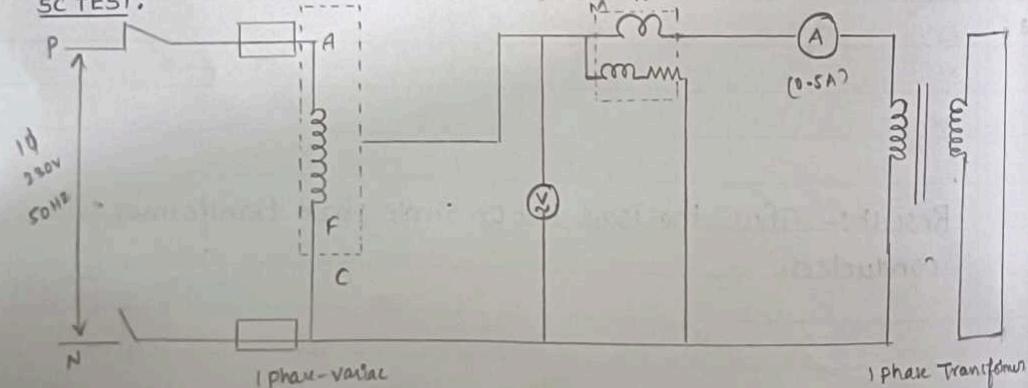


$$P = VI$$


$$P = 24 \times 4.2$$

P = 100 · βW

SA) UPF

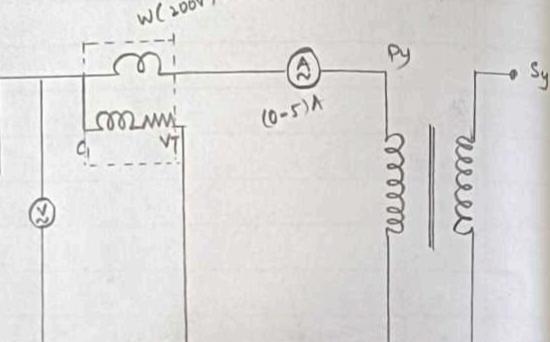

— 1 —

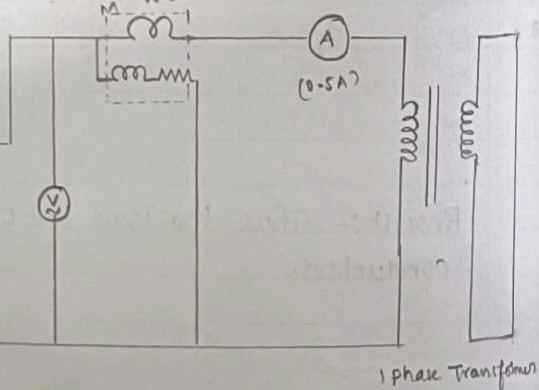

07. OC and SC Test on single phase transformers.

Q1:- To conduct load test on single phase transformers and find the efficiency.

Apparatus Required:-

| S.NO. | APPARATUS Name | Range | Type |
|-------|------------------|--------------|------|
| 1. | Ammeter | 0-10A | MI |
| 2. | Voltmeter | 0-130V | MI |
| 3. | Wattmeter | 300V, 5A | UPR |
| 4. | Auto transformer | 10/ (0-260V) | - |
| 5. | Resistive load | 5KW, 230V | - |

Theory:-


The open circuit and short-circuit tests are essential tests that help to determine the transformer's core losses, copper losses and parameters like equivalent resistance.

procedure :-

1. Connect Voltmeter, ammeter and wattmeter to the primary windings.
 2. Leave the Secondary winding open.
 3. Apply the Voltage and record the readings

Result:- Thus, the OC and SC test on single phase transformers is conducted.

Circuit diagram:-

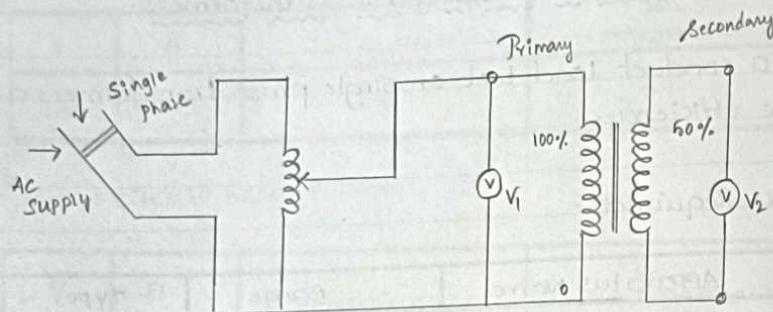

Observation:-

Secondary voltage = 50% of primary voltage.

| S.No. | Primary Voltage (V) | secondary voltage (V) |
|-------|---------------------|-----------------------|
| 1 | 40 | 20 |
| 2 | 60 | 30 |
| 3 | 80 | 40 |
| 4 | 100 | 50 |
| 5 | 120 | 60 |

08. Calculations of secondary Turns and current in a transformer

Aim:- TO Evaluate the secondary turns of current in transformer.

Apparatus Required:-

| S.NO. | Name | Range | Quantity |
|-------|--------------------------|-------------|----------|
| 1. | single phase transformer | 1Φ (0-260V) | 1 |
| 2. | Voltmeter | 0-150V | 1 |
| 3. | Ammeter | 10A | 1 |
| 4. | watt meter | 300V, 5A | 1 |
| 5. | Variable Resistance Load | 5kW, 230V | 1 |

Theory:-


A transformer operates on the principle of electromagnetic induction and consists of the two coils, primary and secondary wound around a common core. When an Ac voltage is applied to the primary coil.

procedure:-

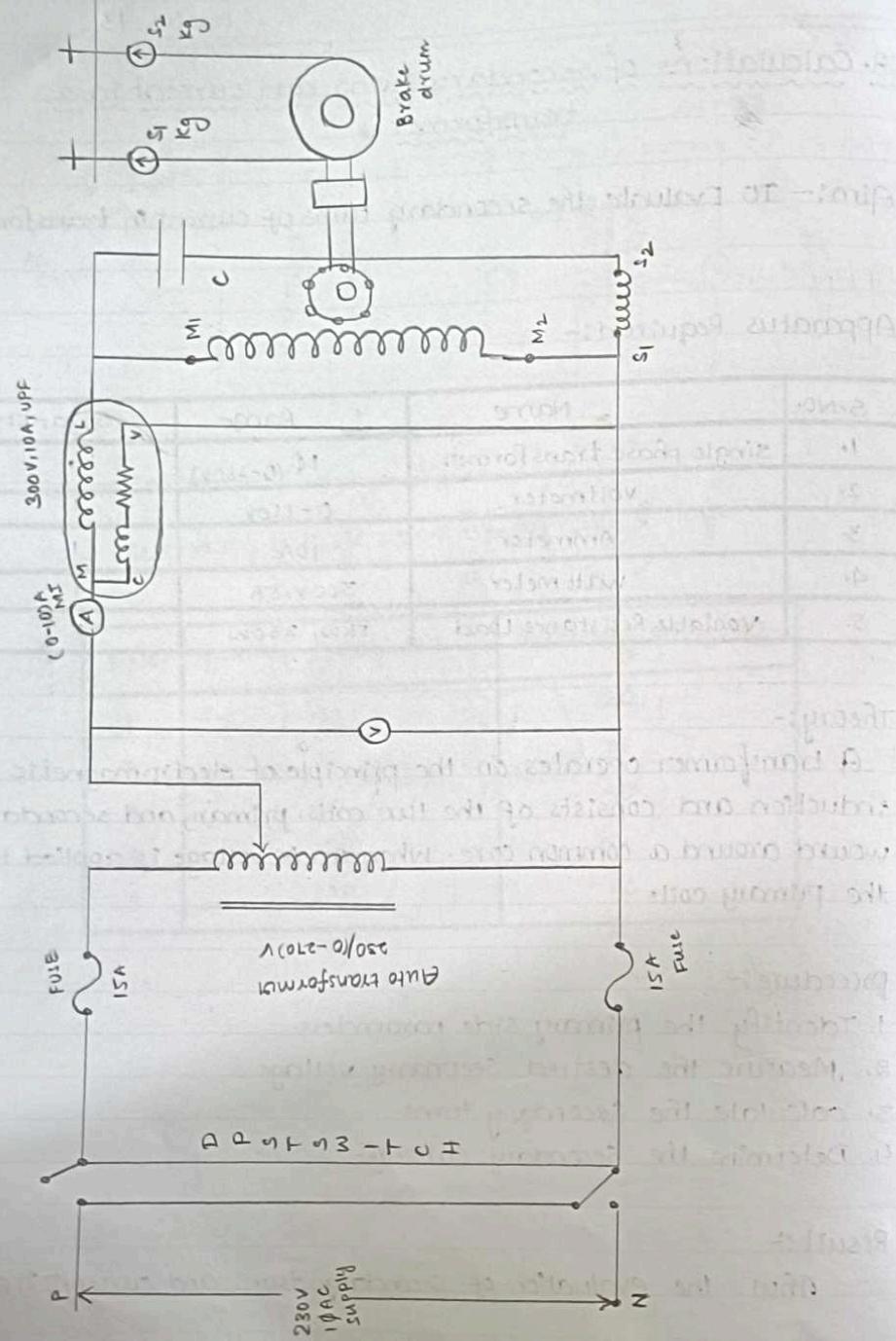1. Identify the primary side parameters.
2. Measure the desired secondary voltage.
3. calculate the Secondary turns
4. Determine the Secondary current.

Result:-

Thus, the evaluation of secondary turns and currents is done.



09. Load test on single phase Induction motor

Aim:- To conduct the load test on the given single phase induction motor and to plot its performance.

Apparatus required:-

| SNO | Apparatus required | Range | Quantity |
|-----|--------------------|--------------|----------|
| 1. | Voltmeter | (0-300V) MI | 1 |
| 2. | Ammeter | (0-10A) MI | 1 |
| 3. | Wattmeter | 300V, 10A | 1 |
| 4. | Tachometer | 10-10000 RPM | 1 |

Theory:-

A load test on a single phase induction motor is performed to evaluate its performance under different load conditions.

Procedure:-

1. Make connections as per diagram.
2. The DPST switch is closed and the single phase supply is given.
3. By adjusting the variance, the rated voltage is applied, no load values of speed, balance and meter readings.
4. The procedure is repeated till rated current of the machine.

Observations:-

| S.No | Volts (V) | Amps (A) | Speed | Watt meter reading | Spring Balance Reading | Torque = $\frac{9 \cdot 81 \times \rho_x}{C_2 - S_1}$ | Output Power = $\frac{2\pi NT}{60}$ | Power factor W/V^2 | $N = \frac{\Omega P}{I^2 P}$ | $S = \frac{Ns - N}{Ns}$ |
|------|-----------|----------|-------|--------------------|------------------------|---|-------------------------------------|----------------------|------------------------------|-------------------------|
| 1 | 230 | 3.2 | 1490 | 300 | 0. | 0 | 0 | 716 | 0 | 0.006 |
| 2 | 230 | 3.6 | 1480 | 540 | 0.8 | 1 | 0.2 | 0.446 | 8.05 | 30.392 |
| 3 | 228 | 4 | 1460 | 760 | 1.6 | 2 | 0.392 | 0.392 | 912 | 59.963 |
| 4 | 226 | 4.5 | 1450 | 900 | 2 | 2.8 | 0.8 | 0.784 | 1017 | 119.106 |

Model Calculations:-

$$T = 9.81 \times 0.1 \times 0.2$$

$$T = 0.1962 \text{ NM}$$

$$\text{Input Power} = 230 \times 3.5 = 850 \text{ W}$$

$$\text{Power out} = 30.392 \text{ W}$$

$$PF = 540 / 230 \times 3.5$$

$$PF = 0.670$$

$$\text{Output Power} = \frac{2 \times 3.14 \times 0.1962 \times 1480}{60}$$

$$\eta = \frac{\Omega}{I} = \frac{30.392}{805}$$

$$\eta = 37.7\%$$

$$\text{Slip} = \frac{1500 - 1480}{1500}$$

$$\text{Slip} = 0.013.$$

Result:- Thus, the performance of DC single phase induction is noted.

Observations:-


| S.NO. | Voltage (V) | Ammeter (A) | watt 1 (W) | watt 2 (W) | Total power (W) |
|-------|-------------|-------------|------------|------------|-----------------|
| 1 | 415 | 2.4 | 688 | 0 | 688 |
| 2 | 415 | 2.5 | 944 | 0 | 944 |
| 3 | 415 | 2.9 | 1112 | 400 | 1512 |
| 4 | 415 | 3 | 1200 | 480 | 1680 |
| 5 | 415 | 3.5 | 1440 | 880 | 2320 |

Calculation:- $W = W_1 + W_2$

$$W = 688 + 0$$

$$W = 688 \text{ W.}$$

Circuit Diagram:-

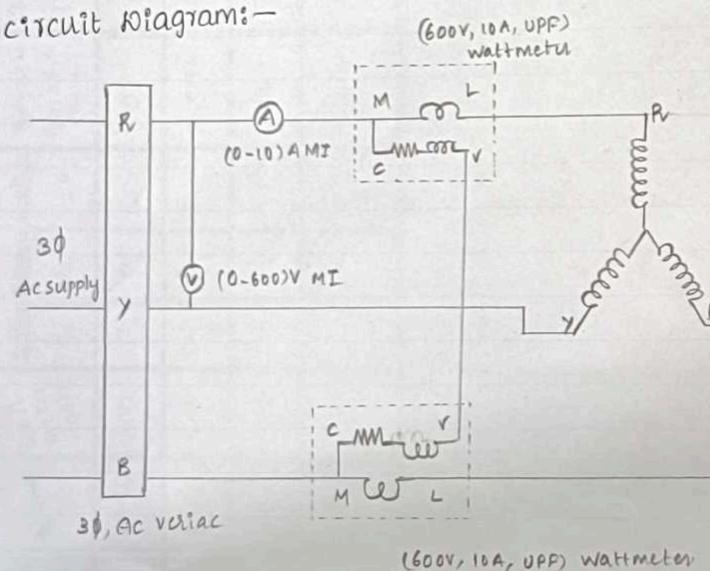

10. Power measurement using TWO WATTMETER METHOD

Aim:- To Evaluate no load parameters in a circuit with open circuit test.

Apparatus Required:-

| S.NO | Name | Range | Quantity |
|------|------------------|---------------|----------|
| 1. | Voltmeter | (0-30)V | 1 |
| 2. | Ammeter | (0-20)A | 1 |
| 3. | Wattmeter | (0-270V) 50Hz | 1 |
| 4. | Auto-Transformer | (0-150) LPF | 1 |
| 5. | Transformer | (CV-115V) | 1 |

Theory:-


This is a popular technique used for measuring power in three phase, three-wired measuring system, especially when dealing with balanced or unbalanced load.

Procedure:-

1. Make the connections as per the circuit diagram.
2. By using 1-phase VARIAC, apply voltage.
3. Measure the voltage and current and power input.

Result:- Thus, the evaluation of no load parameters in a circuit with open-circuit is done.

CIRCUIT DIAGRAM:-

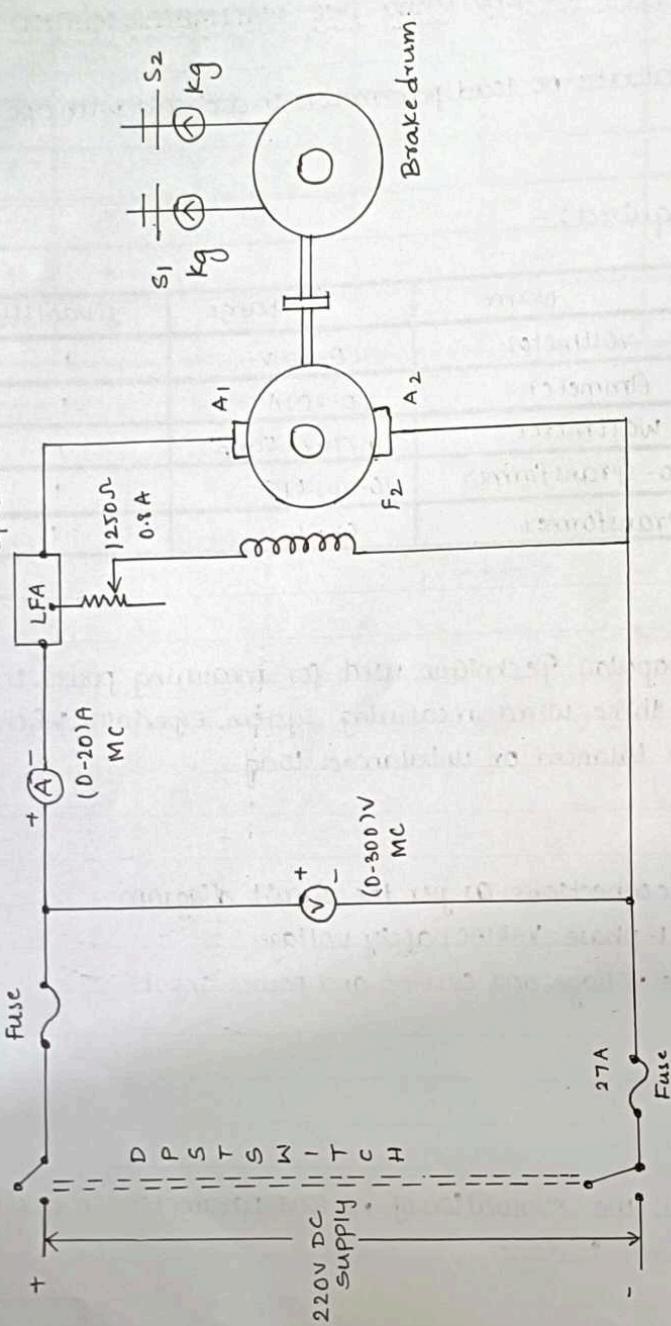

II. Load test on DC SHUNT MOTOR

AIM:— To conduct the brake load test on DC shunt motor and determine its performance.

Apparatus Required:

| S.NO. | Apparatus Name | Range | Quantity |
|-------|------------------|-------------|----------|
| 1. | 220V DC SUPPLY | 0-20 N | 1 |
| 2. | Ammeter | 0-300 A | 1 |
| 3. | Voltmeter | 0-300 V | 1 |
| 4. | Rheostat | 310/1.7 | 1 |
| 5. | RPM meter | (0-199) rpm | 1 |
| 6. | connecting Wires | - | - |

Theory:-

It is a direct method in which a braking force is applied to the pulley mounted on the motor shaft. A belt is wound round the pulley and its turn ends are attached to the frame through two spring balances S₁ and S₂.

Procedure:-

1. make the connections as shown in the circuit diagram.
2. keep the field rheostat at minimum position; switch on the supply.
3. Adjust the speed of the motor ON, NO load to its started value by means of the field rheostat.
4. put on the load by tightening the strings of the spring balances.

OBSERVATION:-

Page No. 18

| S.No | Voltage (V) | Current (A) | Speed (r.p.m) | Spring Balance | | $f_1 = S_1 - S_2 \times 9.81$ $T = F \times R$ (Torque) | Ω/R POWER $V_L \times I_L$ | D/P POWER $2\pi N T / 60$ | Efficiency in % D/P/P _p |
|------|-------------|-------------|---------------|----------------|-------|---|---|---------------------------------|--|
| | | | | S_1 | S_2 | | | | |
| 1 | 220 | 1.6 | 1480 | 0 | 0 | 0 | 352 | 0 | 0 % |
| 2 | 220 | 4 | 1422 | 0.6 | 2.2 | 1.412 | 880 | 210.15 | 23.8 % |
| 3 | 220 | 6 | 1400 | 0.8 | 5.2 | 3.884 | 1320 | 569.135 | 43.1 % |
| 4 | 220 | 8 | 1382 | 1 | 8 | 6.1803 | 1760 | 893.9 | 50.7 % |
| 5 | 218 | 10 | 1378 | 1.2 | 10.2 | 7.946 | 2180 | 1146.05 | 52.5 % |
| 6 | 219 | 12 | 1359 | 1.8 | 18 | 9.88 | 2406 | 1406.4 | 54 % |

CALCULATION:-

$$\begin{aligned} F &= S_1 - S_2 \times 9.81 \\ &= (0.6) - 2.2 \times 9.81 \\ &= (0.6) \times 9.81 \end{aligned}$$

$$F = 15.696$$

$$T = F \times R [R = 0.09]$$

$$P = 15.696 \times 0.09$$

$$P = 1.412 \text{ N-M}$$

$$\begin{aligned} \text{Input power} &= \Omega_L \times V_L \\ &= 40 \times 220 \\ &= 880 \text{ W} \end{aligned}$$

$$\begin{aligned} \text{Output power} &= \frac{2\pi N T}{60} \\ &= \frac{2 \times 3.14 \times 1422 \times 1.412}{60} \\ &= 210.156 \text{ W} \end{aligned}$$

$$\begin{aligned} \text{Efficiency} &= \frac{\text{output power}}{\text{input power}} \times 100 \\ &= \frac{210.156}{880} \times 100 \\ &= 0.23881 \times 100 \\ &= 23.88 \% \end{aligned}$$

Result:- Thus, the performance characteristics of DC shunt motor was obtained by conducting brake test.

OBSERVATION:-


| S.NO | Line voltage V _L (V) | Line current I _L (A) | Time taken for 10 resolutions (sec) | No. of resolution (n) | Energy calculations (kWh) | Measured Energy (kWh) |
|------|------------------------------------|------------------------------------|---|--------------------------|---------------------------------|-----------------------------|
| 1 | 230 | 1 | 85 sec | 10 | 5.43×10^{-3} | 6.66×10^{-3} |
| 2 | 225 | 3 | 38 sec | 10 | 7.125×10^{-3} | 6.66×10^{-3} |

Model Calculations:-

$$\text{Calculated Energy} = \frac{V \times I \times t}{3600} = \frac{5.43}{1000} = 5.43 \times 10^{-3} \text{ kWh.}$$

$$\text{Measured Energy} = \frac{n}{1500 \text{ rev/kWh}} = \frac{16 \text{ rev}}{150 \text{ rev/kWh}} = 6.66 \times 10^{-3} \text{ kWh.}$$

Circuit Diagram:-

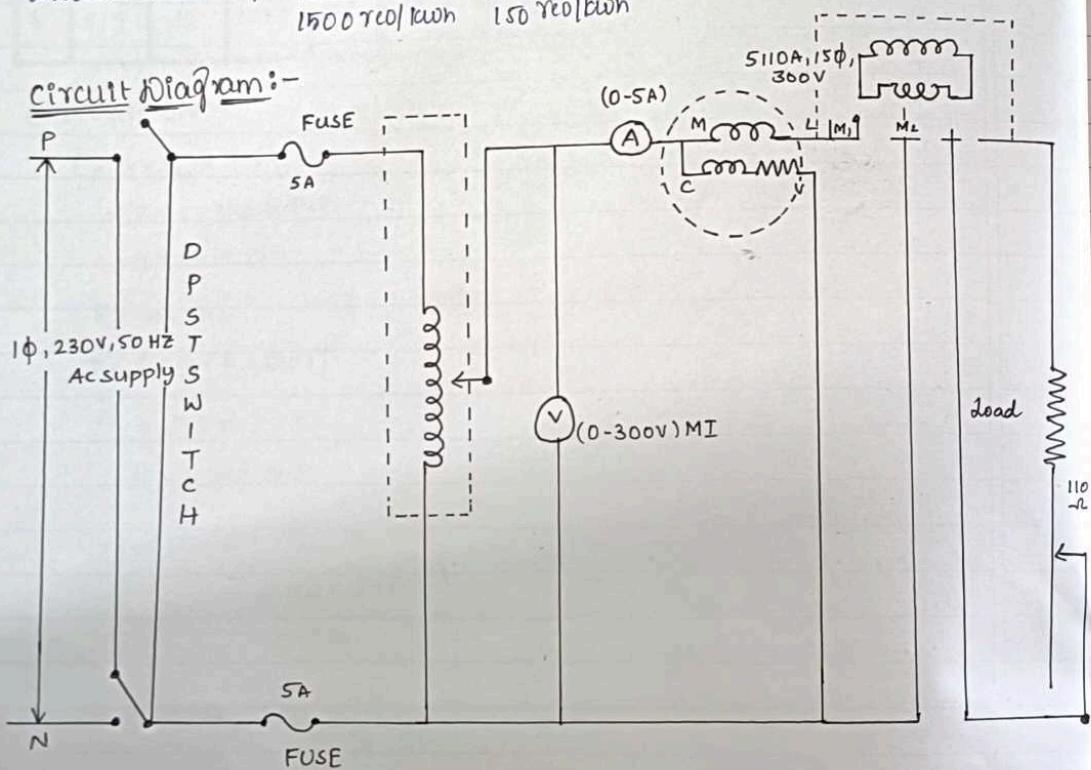

12. Calculation of Energy consumption using Energy Meter.

Aim:- To calibrate and test the given Single phase Energy meter.

Apparatus Required:-

| S.NO. | Name | Range | Quantity |
|-------|--------------------------|---------|-----------|
| 1. | Singlephase Energy Meter | 1500REV | 1 |
| 2. | wattmeter | DPF | 300V |
| 3. | Voltmeter | MI | (0-50)A |
| 4. | Anammeter | MI | (0-5)A |
| 5. | Singlephase Variac | 1-Φ | 230 A |
| 6. | Rheostat | WW | 100Ω, 15A |
| 7. | Stopwatch | - | 1 |

Theory:-


Induction type Of Energy meters are universally used for measuring of Energy in domestic and industrial Ac-circuits. Industrial type of meters possess lower friction and higher torque.

Procedure:-

1. Connection is made as per the circuit diagram.
2. Keep the Single phase variac at zero volt position.
3. Vary the voltage to rated Voltage and variac to zero volt position.
4. Calculate the readings.

Result:- Thus, the given Single phase Energy meter is tested at the different loads.

Circuit diagram:-

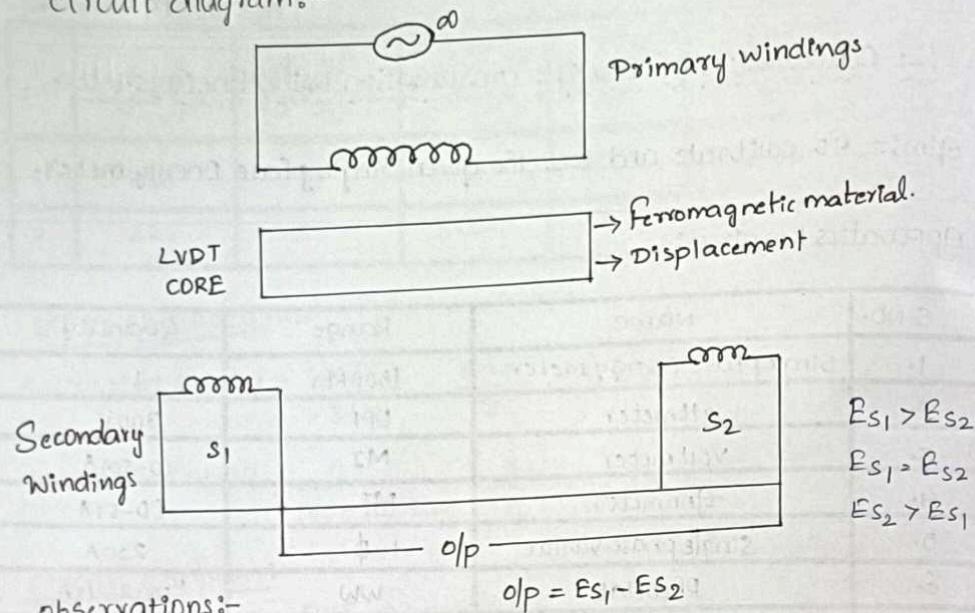

Observations:-

| S.No. | Displacement (mm) | voltage (v) |
|-------|-------------------|-------------|
| 1. | 0 | 5.58 |
| 2. | 1 | 4.95 |
| 3. | 2 | 4.35 |
| 4. | 3 | 3.76 |
| 5. | 4 | 3.11 |
| 6. | 5 | 2.38 |
| 7. | 6 | 1.76 |
| 8. | 7 | 1.00 |
| 9. | 8 | 0.48 |
| 10. | 9 | -0.17 |
| 11. | 10 | -0.85 |

13. Output characteristics of LVDT.

Aim:- To plot the output characteristics of LVDT.

Apparatus Required:-

| S.NO | Name | Quantity |
|------|------------------|----------|
| 1. | LVDT KIT | 1 |
| 2. | MULTIMETER | 1 |
| 3. | CONNECTING WIRES | — |

Theory:-

The linear variable Differential Transformer (LVDT) is an electro-mechanical transformer used to convert linear displacement to an electrical signal.

Procedure:-

1. Connect as per diagram.
2. Switch on the power and make the core null.
3. First turn the nut in clockwise direction, move core inward.
4. Take the readings.

Result:-

Thus, the output characteristics of LVDT is noted.

14 find stability of a system using Routh Hurwitz criterion.

Ques:- To determine the stability of the closed-loop System using Routh Hurwitz criterion.

for: (i) $(s) = s^4 + 2s^2 + 3s^2 + 4s + 5$ and

(ii) $(s) = s^5 + 7s^4 + 6s^3 + 9s^2 + 8s$ and $s6$.

Tools:- SCILAB SOFTWARE & PC.

Program code:-

```
clear;
```

```
clc;
```

```
xdel(winsid());
```

```
mode(0);
```

```
S=%s;
```

$$H = s^4 + s^3 + 3s^2 + 4s + 5;$$

disp(H, "The given characteristics Equations $(1-G(s) + H(s))$ ");

```
C=coeff(H);
```

```
len=length(C);
```

```
r=routh-t(H);
```

```
disp(r, "Routh table=");
```

```
x=0;
```

```
for i=1:len
```

```
if(r(i,1)<0)
```

```
x=x+1;
```

```
end
```

```
end
```


```
if(x>=1)
```

printf("From Routh's table, it is seen that the system is unstable");

```
else
```

printf("From Routh's table, it is evident that the system is stable");



End.

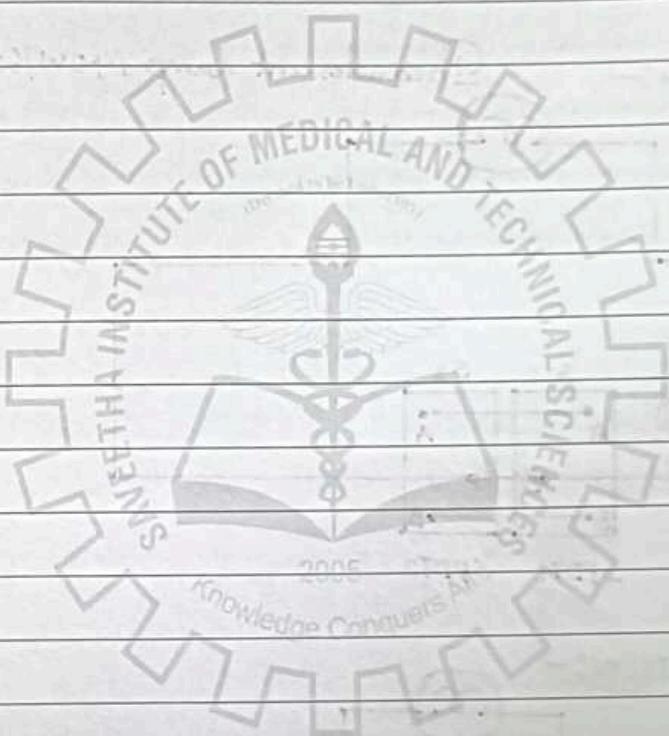

Result:- Thus, the stability of a system using routh hurwitz criterion is verified.

Observation:-Direct connection:-

| SNO | S ₁ | S ₂ | Lamp status |
|-----|----------------|----------------|-------------|
| 1 | CA | C'A' | ON |
| 2 | CB | C'B' | ON |
| 3 | CA | C'B' | OFF |
| 4 | CB | C'A' | OFF |

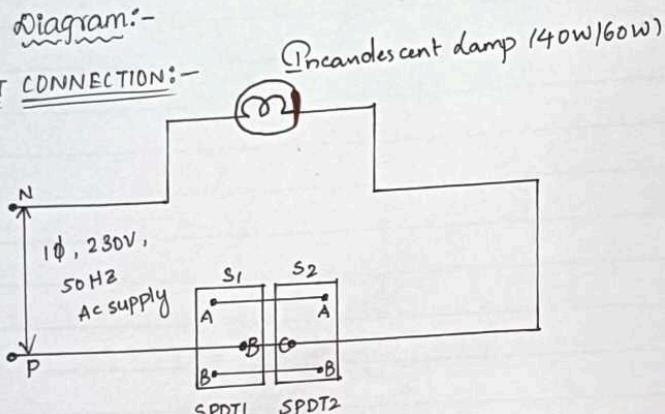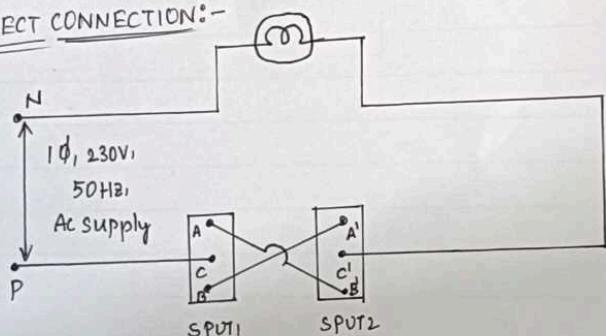Circuit Diagram:-DIRECT CONNECTION:-INDIRECT CONNECTION:-Prdirect connection:-

| S.NO | S ₁ | S ₂ | Lamp status |
|------|----------------|----------------|-------------|
| 1 | CA | C'A' | OFF |
| 2 | CB | C'B' | OFF |
| 3 | CA | C'B' | ON |
| 4 | CB | C'A' | ON |

15. STAIRCASE WIRING

(a.)

Aim:- To control the status of the lamp using a two-way switch.

Apparatus required:-

| S.NO. | Name | Range | Quantity |
|-------|--------------------------|--------------|----------|
| 1. | Incandescent lamp | 60W/40W | 1 |
| 2. | SPDT, Throw 2-way switch | 5A, 230V | 2 |
| 3. | Lamp holder | Pendant type | 1 |
| 4. | dine pester | 500V | 1 |
| 5. | 3 pin plug | 5A, 230V | 1 |
| 6. | wire stripper | PYE 950 | 1 |

Theory:-

Staircase wiring is a common multi-way switching connection where one lamp is controlled by 2-switches from two different positions that is to operate from above the stairs and below.


Procedure:-

1. A wire is connected to the phase side and other side to the mid point of SPDT switch.
2. Another point of lamp holder is connected to the neutral wire.
3. Upper point of SPDT switch is connected to switch 2 and lower point of switch 2 to switch 1.

Result:-

Thus, the given lamp was controlled by direct and indirect connections using 2-way switches.

Circuit diagram:-

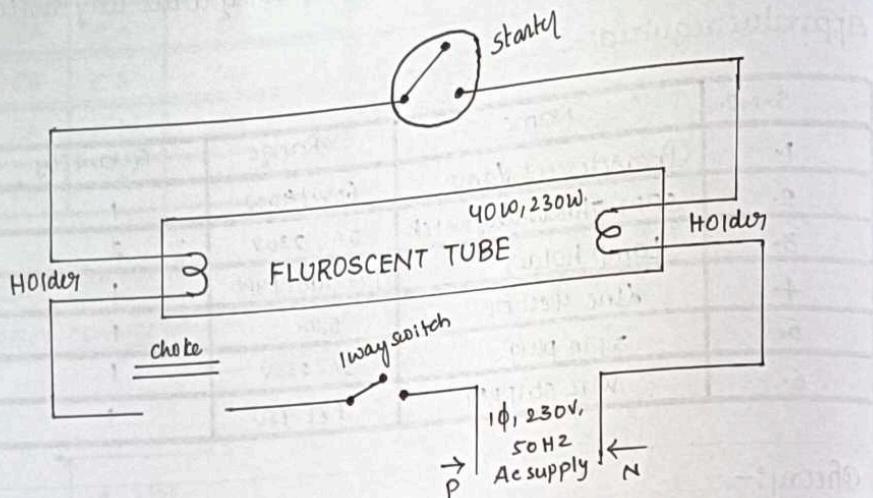

15 • FLUORESCENT TUBE WIRING.

(b).

Aim:- To prepare wiring for a fluorescent tube light with switch control.

Apparatus Required:-

| S.NO. | Name | Quantity |
|-------|-------------------------|----------|
| 1. | Pubelight with fittings | 1 |
| 2. | Joint clips & wires | Required |
| 3. | Switch | 1 |
| 4. | Screws | Required |

Theory:-

The fluorescent lamp circuit consists of a choke, a starter, a fluorescent tube of the commonly used fluorescent tube is 100cm.

Procedure:-

1. Draw the wires on the wooden board.
2. place the wires on the lines and fix with clips.
3. fix switch & tube light in marked positions.
4. complete wirings as per diagram.

Result:-

Thus, the wiring for the tube light is completed and also tested.

16. Generation of common discrete time signals.

Aim:- To Generate impulse signals, unit step signals, unit Ramp signals, Sinusoidal signals and Exponential signals.

software required:- scilab 6.1.0

procedure:-

1. Start the scilab program
2. open scinotes , type the program & save it.
3. Compile & Run the program
4. Stop the program

Theory:-

Unit step signals $v[n]$:- It is a basic discrete time signal that takes the value 1 for $n \geq 0$ & 0 for non-negative time indices.

Impulse signal :- Also known as the discrete-time delta function. It has a value of 1 at $n=0$ & 0 for other indices.

Exponential signals:- Defined as $x[n] = A * d^n$, where A is amplitude, d is Exponential factor and depending on whether d is greater or less than 1, the signal grows or decays.

Sinusoidal signals:- It has the form $x[n] = A * \cos(\omega n + \phi)$, where A is amplitude, ω is angular frequency & n is time.

program:-

unit step:

```
t = -5:0.1:5;
```

```
y = zeros(1, length(t));
```

```
y(t>=0) = 1;
```

```
plot(t,y, "line-width", 2);
```

```
xlabel("time (t)");
```

```
ylabel("u(t)");
```

Exponential:

```
t = 0:0.1:10;
```

```
x = exp(t);
```

```
plot(t,x);
```

```
title("Exponential wave");
```

```
xlabel('t');
```

```
ylabel('x');
```

RAMP:

```
t = 0:0.1:10;
```

```
ramp = t;
```

```
plot(t,ramp);
```

```
xlabel("time (t)");
```

```
ylabel("Amplitude");
```

Impulse:

```
t = -5:0.1:5;
```

```
impulse = zeros(t);
```

```
impulse(t=0) = 1;
```

```
plot(t,impulse);
```

```
xlabel("Time");
```

```
ylabel("Amplitude");
```

Sinusoidal:

```
f = 500/;
```

```
t = 0:0.001:0.02;
```

```
x = sin(2*pi*f*t);
```

```
plot(t,x);
```

```
xlabel('t');
```

```
ylabel('x');
```

Result:-

Thus, the discrete-time signals were successfully generated.

17. DIT-FFT & DIF-FFT ALGORITHMS.

[a]. DIT-FFT:-

Ques:- To compute the DFT for sequence

$$x[n] = [1, -1, -1, -1, 1, 1, 1, 1, -1] \text{ using DIT-FFT Algorithm.}$$

Software Required: Scilab 6.1.0.

procedure:-

1. start the scilab program
2. open scinotes & type the program
3. compile and run the program
4. observe and record output, stop the program.

Theory:

The decimation in-time fast fourier transform (DIT-FFT) algorithm is a method to compute the discrete fourier transformation of a sequence.

$$X[k] = \sum_{n=0}^{N-1} x[n] e^{-j \frac{2\pi k n}{N}}, \quad (N = 0, 1, 2, \dots, N-1)$$

program:-

clear;

clc;

close;

$x = [1, -1, -1, -1, 1, 1, 1, 1, -1];$

$X = fft(x, -1);$

$disp(X, X'(z) = 1);$

Result:-

Thus, the DFT for the given sequence is implemented and observed.

17.

[b]. DIF-FFT:-

Ques:- Q0 compute the DFT of the sequence

 $x[n] = [1, 2, 3, 4, 4, 3, 2, 1]$ using the decimation-in frequency FFT.

procedure :-

1. Start the scilab program.
2. Open scinotes and type the code.
3. Compile & Run the program.
4. Observe the output & Stop the program.

Theory:-

DIF-FFT Algorithm is used for computing the discrete fourier transformation (DFT) . complexity is Expressed.

$$X[k] = \sum_{n=0}^{N-1} x[n] \cdot e^{-j \frac{2\pi}{N} kn}, k = 0, 1, 2, \dots, N-1$$

Program:-

clear;

clc;

close;

 $x = [1, 2, 3, 4, 4, 3, 2, 1];$

//FFT computation

 $X = \text{FFT}(x, -1);$

disp(x, X'(z) = 1);

Result:-

Thus, the DFT of the sequence $x[n] = [1, 2, 3, 4, 4, 3, 2, 1]$ using DFT-FFT algorithm.

18. Bilinear and Impulse invariant Transform.

[a]. Bilinear:-

Aim:- To convert the continuous-time analysis transfer function $H(s) = s^2 + 4.525s^2 + 0.692s^2 + 0.504$ into discrete time transfer function using bilinear transformation.

procedure:-

1. Start the scilab program.
2. openscicones and type the program
3. Compile and Run the program.
4. Records the output and stop the program.

Theory:-

The digital signal processings conversion, an analog filter design into discrete filter which is crucial for implementing filters.

program:-

clear;

clc;

close;

$S = -j\omega$;

$Z = e^{j\omega T}$;

$$H_z = (S^2 + 4.S) / (S^2 + 0.692 \times S + 0.504);$$

$T = 1;$

$$Hz = horur(Hz, (2/T) * (Z-1)/(Z+1));$$

disp (Hz, 'H(z)=1');

Result:-

Thus, DTTF is obtained after apply the bilinear transformation

18. [b]. Impulsive Invariant transformation.

Aim:- To convert the continuous time, analog transfer functions:

$H(s) = 10/(s^2 + 7s + 10)$ into discrete time digital transfer function.

Procedure:-

1. Start the scilab program.
2. Open the scinotes & type the program.
3. Compile & Run the program.
4. Record the output & exit.

Program:-

clear;

clc;

close;

$s = %i * \pi$

$T = 0.2$

$$Hs = 10/(s^2 + 7s + 10);$$

$$e Hs = pfss(Hs);$$

$$\text{disp}(e.Hs, 'Factorized Hs = ');$$

$$P1 = -5;$$

$$P2 = -2;$$

$$z = \% Z;$$

$$Hz = T * ((-3.33)(1 - \% e^{(P1 * T)} * z^n(-1)) + (3.33 / (1 - \% e^{(P2 * T)} * z^n(-1)));$$

$$\text{disp}(Hz, 'Hz = ');$$

$$Ts = 0.01;$$

$$S = tf('s');$$

$$sys = (10/s^2 + 7s + 10);$$

$$\text{sysd} = c2d(sys, Ts, zoh)$$

$$tf(Sysd)$$

$$\text{step}(Sysd, 10)$$

Guidon

Result:-

Thus the discrete time transfer function is obtained.

19 • Analog Butterworth filter.

[a]:

Aim:- To design a butterworth filter for processing auto signals that alternates frequencies above 0.2.

Procedure :-

1. open the scilab software
2. open scinotes & type the program & compile
3. Record the output and Exit.

Theory:-

The butter worth low pass filter is most used type of analog filter that is known for its maximum frequency response.

Program:-

```

clear;
clc;
close
s=poly(0,'s');
omegac = 0.2 * %pi;
H=omegac/(s+omegac);
z=poly(0,'z');
w=0.1*pi/5*pi:1*pi;
plot(w,abs(H),H)
a=grca();
xgrid(0)
disp("Hz", Hz);

```

Result:- Thus, the butter worth filter has successfully altered frequencies above 0.2

15 [b]

Aim:- To design a butter worth high-pass filter for a digital audio process.

Software Required: scilab 6.1.0

Procedure:-

1. Start the scilab program
2. Open scinotes, type the program and compile it.
3. Record the output and Exit.

Program:-

```

clear;
clc;
close;
s = poly(0,'s');
Omega = 0.2 * %pi;
T = 1;
H = Omega / (s + Omega);
z = poly(0, 'z');
Hz_LPF = horner(H, (2/T) * ((z - 1) / (z + 1)));
alpha = - (cos(Omega) + Omega) / (2);
Hz_PH = horner(Hz_LPF, -(z + alpha) / (1 + alpha * z));
HW = 0 : %pi / 511 : %pi;
a = g(a0);
a, thickness = 1;
xtitle = "(magnitude response of single pole HPF filter";
xtitle = "magnitude)";


```

Result:- Thus, the butter worth high-pass filter for a digital audio process is successfully designed & Executed.

Tabulation:-

| F (f) | V (V) | Ratio N _s = $\frac{120f}{P}$ | RPM | Gauge slip meter ppm | No. of poles | Synchronous speed@50Hz | Synchronous speed@60Hz | |
|----------|----------|--|-------|-------------------------------|--------------|---------------------------|---------------------------|------|
| 8.6 | 40 | 4.6 | 258.6 | 250 | 0.033 | 2 | 3000 | 2600 |
| 12.5 | 56 | 4.5 | 370.8 | 310 | 0.012 | 4 | 1100 | 1800 |
| 14.5 | 65 | 4.4 | 436.5 | 436 | 0.01 | 6 | 1000 | 1400 |
| 18.2 | 82 | 4.4 | 548.7 | 548 | 0.001 | 8 | 900 | 900 |
| 23.7 | 106 | 4.4 | 713.1 | 713 | 0.0001 | 12 | 500 | 600 |

Circuit Diagram:-

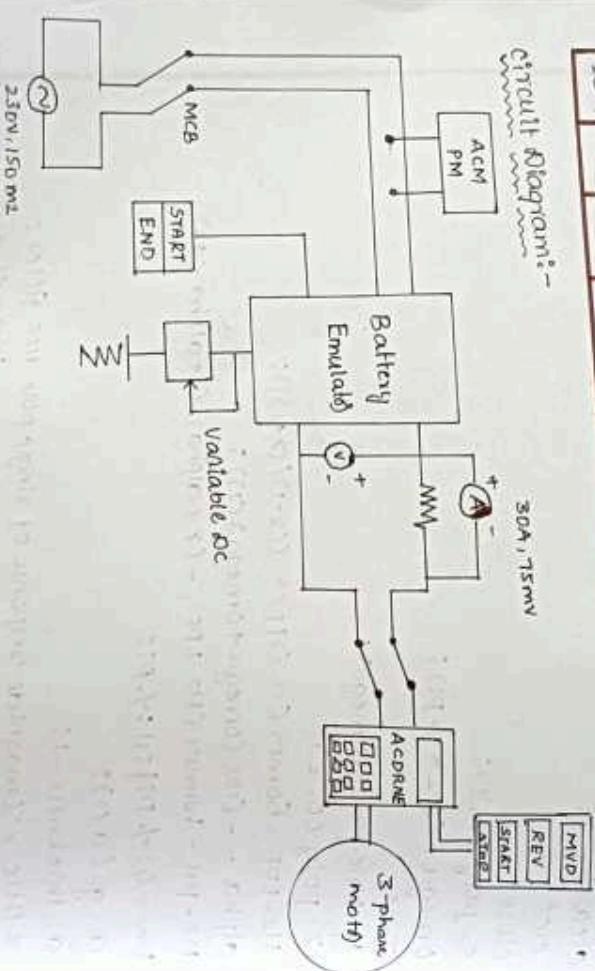

20. THREE-PHASE INDUCTION MOTOR DRIVE SYSTEM

Aim :- To study the function of three-phase induction motor drive system in auto mobile.

Apparatus Required:-

| S.NO. | Name | Quantity |
|-------|---|----------|
| 1. | Three phase Induction motor | 1 |
| 2. | Panel with DC Voltmeter, DC ammeter, AC ammeter | 1 |
| 3. | Battery Emulator | 1 |
| 4. | Human Machine Interface | 1 |
| 5. | 12V Alternating batteries for load | 1 |

Procedure:-

- Give the AC supply to meter [5]. Battery Emulator
- Putly rotate potentiometer of a.c control
- Select forward mode using upo
- Vary the frequency using vfo
- Calculate the different values given

Caution:-

- dont connect overload supply
- check proper connection
- Dont overload motor

Result:-
Thus, functions of three phase Induction motor drive system is observed successfully.